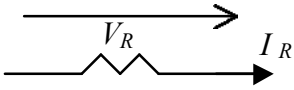
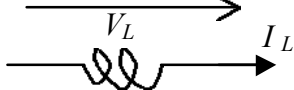
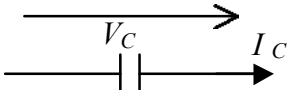
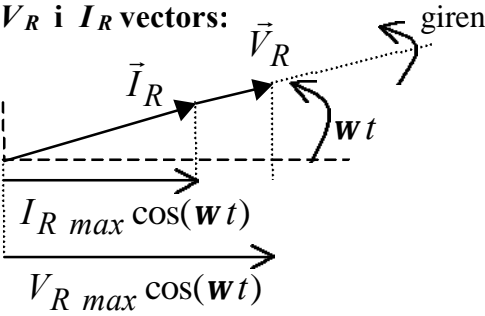
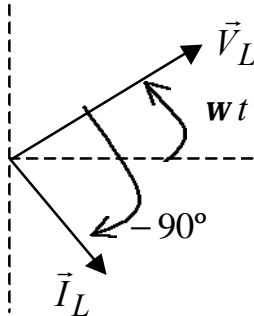
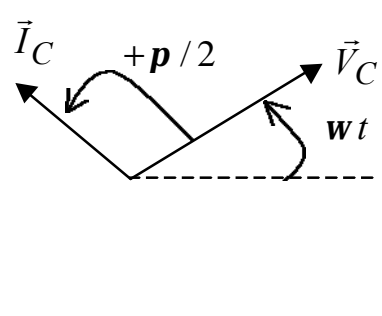


CORRENT ALTERN (Components bàsics)

Resistència	Bobina	Condensador
		
<p>Si $V_R = V_{Rmax} \cos(\omega t)$</p> $I_R = \frac{V_R}{R} = I_{Rmax} \cos(\omega t)$ $I_{Rmax} = \frac{V_{Rmax}}{R}$	<p>Si $V_L = V_{Lmax} \cos(\omega t)$</p> $I_L = I_{Lmax} \cos\left(\omega t - \frac{p}{2}\right)$ $I_{Lmax} = \frac{V_{Lmax}}{X_L} = \frac{V_{Lmax}}{L\omega}$	<p>Si $V_C = V_{Cmax} \cos(\omega t)$</p> $I_C = I_{Cmax} \cos\left(\omega t + \frac{p}{2}\right)$ $I_{Cmax} = \frac{V_{Cmax}}{X_C} = \frac{V_{Cmax}}{1/(C\omega)}$
<p>Podem associar a V_R i I_R vectors:</p> 		
<p>Podem associar a V_R i I_R complexes:</p> $\bar{I}_R = I_{Rmax} \langle \omega t$ $\bar{V}_R = V_{Rmax} \langle \omega t$ <p>Parts reals:</p> $\text{Re}(\bar{I}_R) = I_{Rmax} \cos(\omega t) = I_R$ $\text{Re}(\bar{V}_R) = \dots = V_R$	$\bar{I}_L = I_{Lmax} \langle \omega t - \frac{p}{2}$ $\bar{V}_L = V_{Lmax} \langle \omega t$ $\text{Re}(\bar{I}_L) = I_{Lmax} \cos\left(\omega t - \frac{p}{2}\right)$ $\text{Re}(\bar{I}_L) = I_L$ $\text{Re}(\bar{V}_L) = \dots = V_L$	$\bar{I}_C = I_{Cmax} \langle \omega t + \frac{p}{2}$ $\bar{V}_C = V_{Cmax} \langle \omega t$ $\text{Re}(\bar{I}_C) = I_{Cmax} \cos\left(\omega t + \frac{p}{2}\right)$ $\text{Re}(\bar{I}_C) = I_C$ $\text{Re}(\bar{V}_C) = \dots = V_C$
$\bar{I}_R = I_{Rmax} \langle \omega t = \left(\frac{V_{Rmax}}{R}\right) \langle \omega t$ $\bar{I}_R = \frac{(V_{Rmax}) \langle \omega t}{R \langle 0^\circ} = \frac{\bar{V}_R}{R}$	$\bar{I}_L = \left(\frac{V_{Lmax}}{X_L}\right) \langle \omega t - \frac{p}{2}$ $\bar{I}_L = \frac{V_{Lmax} \langle \omega t}{X_L \langle \frac{p}{2}} = \frac{\bar{V}_L}{\bar{X}_L}$	$\bar{I}_C = \left(\frac{V_{Cmax}}{X_C}\right) \langle \omega t + \frac{p}{2}$ $\bar{I}_C = \frac{V_{Cmax} \langle \omega t}{X_C \langle -\frac{p}{2}} = \frac{\bar{V}_C}{\bar{X}_C}$
<p>Definim la impedància $\bar{Z} = \bar{V} / \bar{I}$:</p> $\bar{Z}_R = \frac{\bar{V}_R}{\bar{I}_R} = R = R \langle 0^\circ = R + 0j$ <p style="text-align: center;">($j = \sqrt{-1}$)</p>	$\bar{Z}_L = \frac{\bar{V}_L}{\bar{I}_L} = \bar{X}_L = X_L \langle \frac{p}{2}$ $\bar{Z}_L = 0 + jX_L = jX_L = jL\omega$	$\bar{Z}_C = \frac{\bar{V}_C}{\bar{I}_C} = \bar{X}_C = X_C \langle -\frac{p}{2}$ $\bar{Z}_C = 0 - jX_C = -jX_C = \frac{-j}{C\omega}$